

# **Project Report Submission**

*For*

## **Digital IC Design**

*(ELE4620)*

**Title: Design a Full adder using CMOS transistor**

*Submitted By*

**Munazir Reza (20ELB172)**

*Submitted To*

**Dr. Mohammad Wajid**

*Submission Date: 20-11-2023*

# Abstract

This study presents the design and implementation of a Full Adder circuit using CMOS transistor technology. The Full Adder is a fundamental component in digital circuits, crucial for arithmetic and logical operations. Leveraging CMOS technology, this research focuses on optimizing the circuit's performance metrics, such as speed, power efficiency, and area utilization. The Full Adder design is realized through the integration of complementary Metal-Oxide-Semiconductor (CMOS) transistors, utilizing their inherent advantages in terms of low power consumption, high noise immunity, and compatibility with integrated circuit manufacturing processes. Simulation and analysis are conducted using Cadence Virtuoso tools to assess the circuit's functionality, performance parameters, and scalability across different process nodes. The findings and insights from this study contribute to advancing the understanding and application of CMOS-based Full Adder circuits in modern digital systems.

## Design step

### Step 1: Design half Adder using CMOS transistor.

Figure 1 shows the schematic of half adder comprises XOR, Inverter, AND gate

$$\text{Sum} = A \oplus B \quad \text{---(1)}$$

$$\text{Carry} = A \cdot B \quad \text{----(2)}$$

Where A & B are inputs and sum & carry are outputs

Truth Table for Half Adder

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

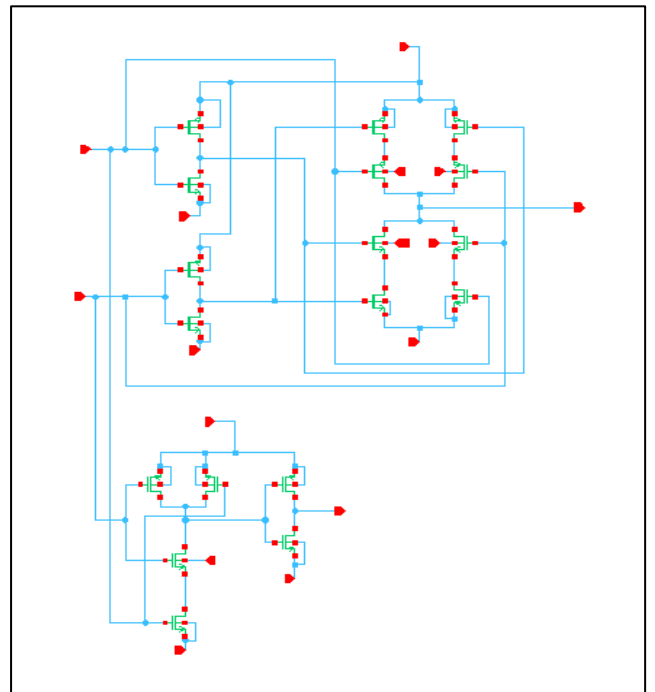


Figure 1 Half Adder

### Step 2: Half adder Layout

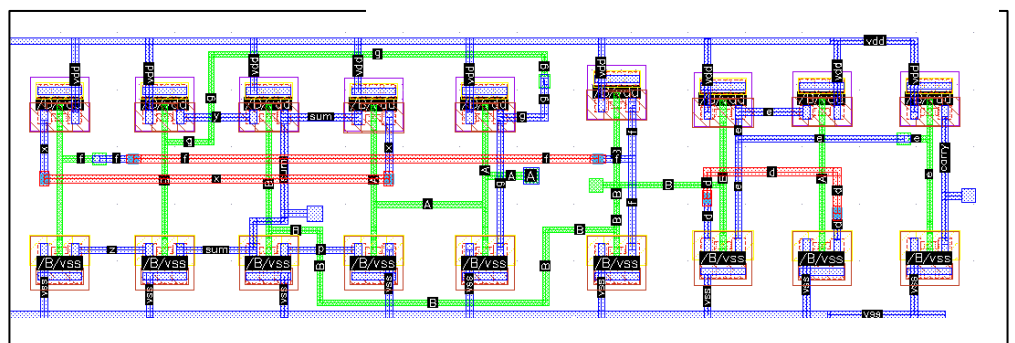


Figure 2 Half adder layout

### Step 3: DRC Check (No DRC found )

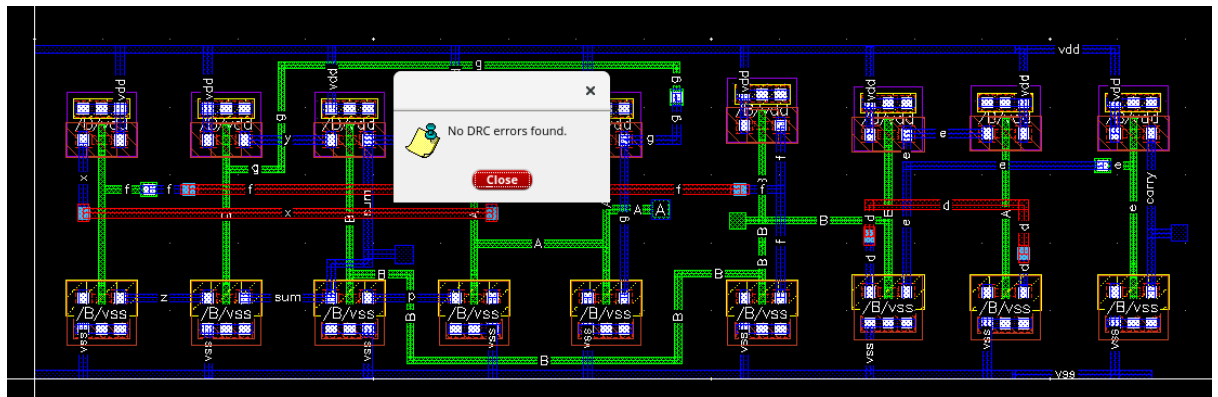


Figure 3 DRC Checking

### Step 3: Half adder av extracted

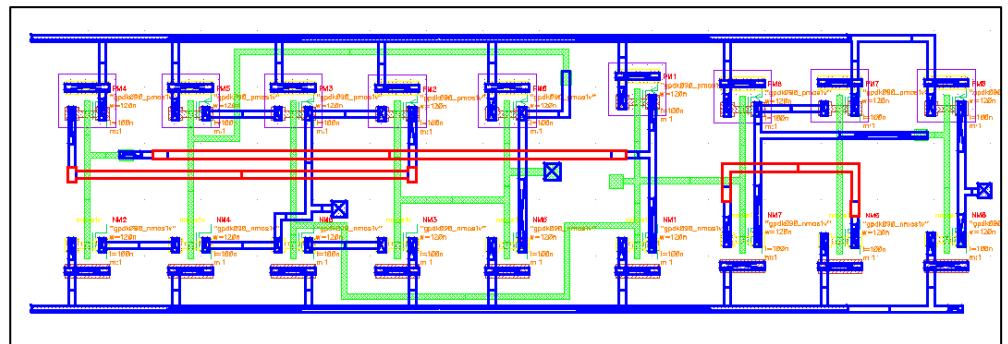


Figure 4 av-extracte view

### Step 4: Data stream (GDS file)

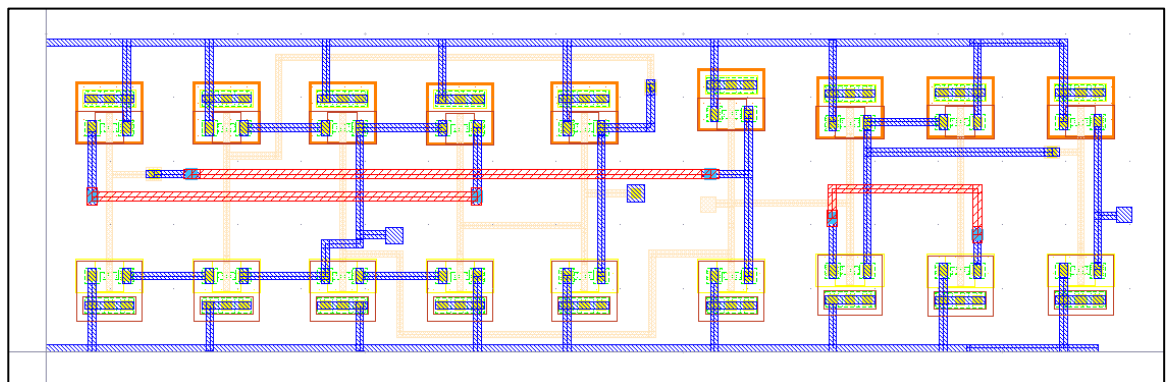


Figure 5 GDS extracted view

### Step 5: Half Adder Testbench

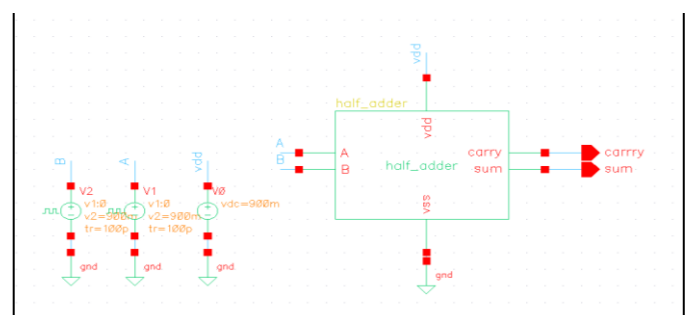


Figure 6 Half Adde Testbench

## Step 6: Half Adder Waveform

 


Figure 7 Half Adder Waveform

## Step 7: OR Gate Schematic

OR gate Truth table

$$Y = A \text{ or } B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

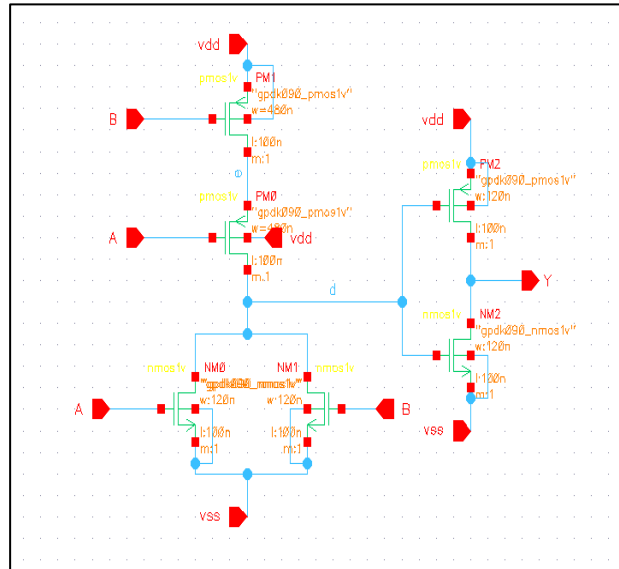


Figure 8 OR Gate Schematic

## Step 8: Half Adder Layout

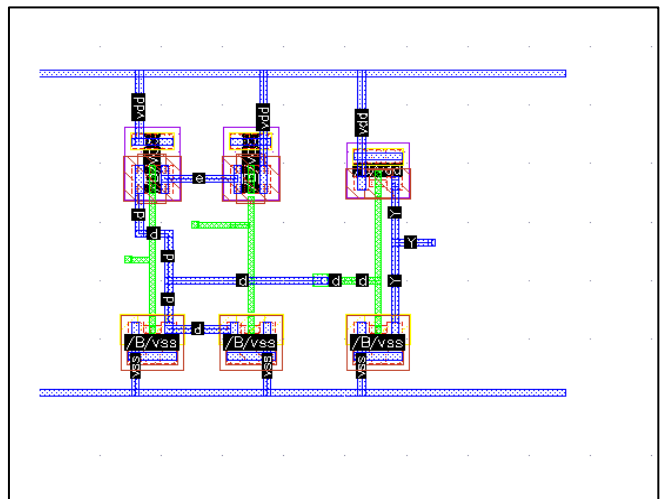


Figure 9 OR Gate Layout

## Step 9: DRC Check

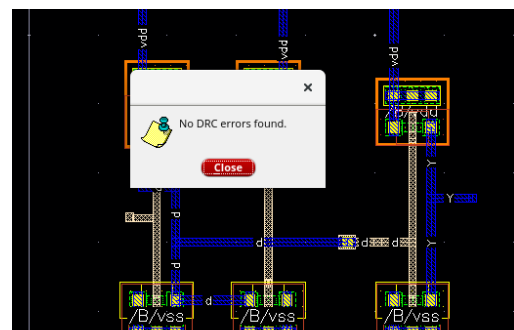


Figure 10 RDC View

A circuit diagram of an OR gate. The gate is represented by a green symbol with a curved input side and a pointed output side. There are four input lines: two on the left labeled 'A' and 'B' in red, and two on the top and bottom labeled 'vdd' and 'vss' in red. The output line on the right is labeled 'Y' in red. The text 'or\_gate' is written in yellow twice, once near each of the left inputs. The entire diagram is overlaid on a light gray grid.

Figure 13 OR Gate Testbench

### Step 13: OR Gate Waveform

 


Figure 14 OR Gate waveform

### Step 14: Full Adder Block Diagram using HA & AND gate

$$\text{Sum} = A \oplus B \oplus \text{cin}$$

$$\text{Carry} = A.B + B.\text{Cin} + A.\text{Cin}$$

A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

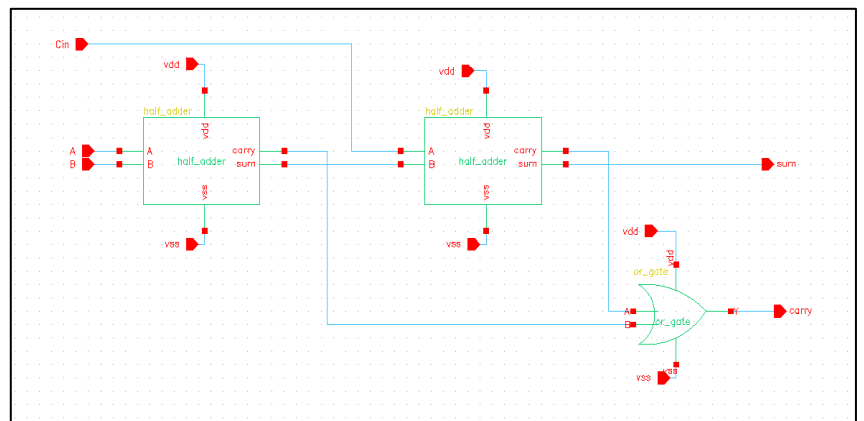


Figure 15 Full Adder Block Diagram

### Step 15: Full Adder layout

 


Figure 16 Full Adder Layout

### Step 16: Full Adder Data stream (GDS)

 


Figure 17 Full Adder GDS View

## Step 17: Full Adder Testbench

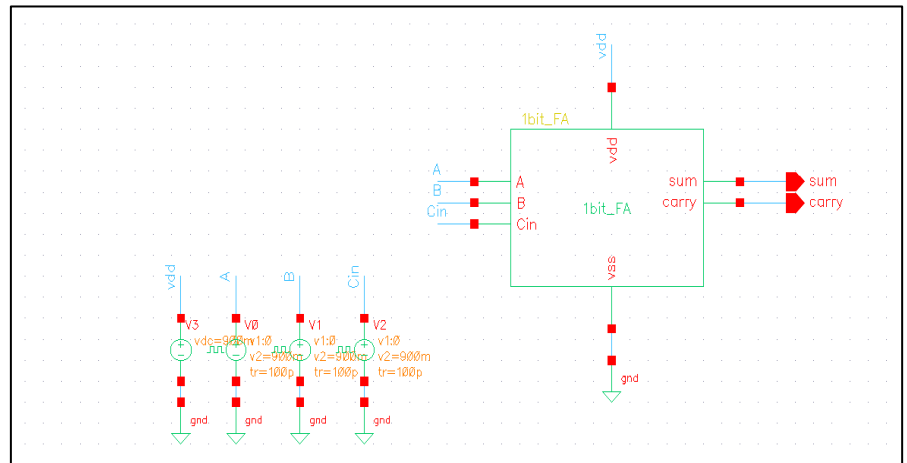


Figure 18 Full Adder Testbench

## Step 18: Full Adder Waveform


 



Figure 19 Full Adder Waveform

## Static and Dynamic Power


### 1. OR gate

 

## 2. Half adder

 

## 3. Full Adder

 

## Delay Calculation

1. Delay between input A and sum for full adder is  $158.9 \times 10^{-12}$  sec

## Discussion

We've successfully implemented the schematic and layout designs for a half adder, an AND gate, and a full adder. Additionally, we verified the waveform output against the truth table. Following this, we conducted checks for Design Rule Checking (DRC) errors and extracted



RC parameters, generating a data stream. We performed calculations for both Static and Dynamic power, alongside measuring the delay for one input of the full adder